

LAB REPORT

*****On Numbers and Display*****

Author 洪晨辉 3220101111

Date 2024.12.3

1. Problem Description

1) Design a 4-to-2 bit binary to BCD digital circuit using the certain structure provided in the FPGA guidance. Display it through two seven-segment display.

2) Make a 2 digit BCD adder.

3) There's a specific ingenious way to implement a 2 digit BCD adder with logic provided below. Try it out.


1 $T0 = A0 + B0$ 2 if $(T0 > 9)$ then 3 $Z0 = 10$; 4 $c1 = 1$; 5 else 6 $Z0 = 0$; 7 $c1 = 0$; 8 end if 9 $S0 = T0 - Z0$ 10 $T1 = A1 + B1 + c1$ 11 if $(T1 > 9)$ then 12 $Z1 = 10$; 13 $c2 = 1$; 14 else 15 $Z1 = 0$; 16 $c2 = 0$; 17 end if 18 $S1 = T1 - Z1$ 19 $S2 = c2$

4) Upgrade the 4-to-2 BCD conversion circuit into 6 bit one.

 2. Design Formulation

Part II

As much as I love to, the guidance has pose restrictions on circuit design. It must consist of the following structure,



Which means the circuit must consists of these stuff,

Comparator: determines if the 4-bit binary input is greater than 3.

Circuit A and B: Adjust value for Ones or Tens.

Seven-segment decoder: You know the drill.

Part V

Theoretically, one should implement many adders and such. But for us lazy-bones, we just use some plus operand tips-and-tricks provided by IEEE standard library anyway. Not a big deal.

Part VI

Yay, we have if-else block now. Just copy and paste it and we'll be fine.

Part VII

Nah, the method provided by Part II is dumb. Why do those structural stuff when you could easily pull out the truth table implementation in your sleeve, and completely wrench the well-organized design into a deep abyss of horribly strangled logic gates? But hey, what do you expect? It's convenient! So don't judge me.

Truth table as follows,

Truth Table for 6-Bit Binary to BCD

Binary Input (6-bit)	Decimal Value	BCD Tens (MSB)	BCD Ones (LSB)
000000	0	0000	0000
000001	1	0000	0001
000010	2	0000	0010
000011	3	0000	0011
000100	4	0000	0100
000101	5	0000	0101
000110	6	0000	0110
000111	7	0000	0111
001000	8	0000	1000
001001	9	0000	1001
001010	10	0001	0000
001011	11	0001	0001
...
111110	62	0110	0010
111111	63	0110	0011

This table directly maps every 6-bit binary input to its equivalent BCD output.

3. Design Entry

Part II

Part2.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity part2 is
5.     Port (
6.         sw : in STD_LOGIC_VECTOR(3 d
7.             own to 0); -- 4-bit binary input
8.         hex1,hex0 : out STD_LOGIC_VECTOR(7
9.             downto 0)
10.    );
11. end part2;
12.
13. architecture Structural of part2 is
14.     -- Signals
15.     signal z : STD_LOGIC; -
16.         - Comparator result
17.     signal bcd_tens : STD_LOGIC; --
18.         BCD tens digit
19.     signal bcd_ones : STD_LOGIC_VEC
20.         TOR(3 downto 0); -- BCD ones digit
21.
22. begin
23.     -- Instantiate Comparator
24.     COMP: entity work.Comparator4
25.         Port Map (
26.             binary_in => sw,
27.             z => z

```

```

23.         );
24.
25.     -- Instantiate Circuit A (Ones)
26.     CIRCA: entity work.CircuitA4
27.         Port Map (
28.             binary_in => sw,
29.             z => z,
30.             bcd_ones => bcd_ones
31.         );
32.
33.     -- Instantiate Circuit B (Tens)
34.     CIRCB: entity work.CircuitB4
35.         Port Map (
36.             z => z,
37.             bcd_tens => bcd_tens
38.         );
39.
40.     HEX_1: entity work.char_7segB
41.         Port Map (
42.             c => bcd_tens,
43.             display => hex1
44.         );
45.
46.     HEX_0: entity work.char_7seg
47.         Port Map (
48.             c => bcd_ones,
49.             display => hex0
50.         );
51.
52. end Structural;

```

Comparator4.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity Comparator4 is
5.     Port (
6.         binary_in : in STD_LOGIC_VEC
7.             TOR(3 downto 0); -- 4-bit binary inp
8.             ut
9.         z : out STD_LOGIC --
10.             High if binary_in >= 10
11.    );
12. end Comparator4;

```

```

10.
11. architecture PureLogic of Comparator
    4 is
12. begin
13.     -- z = 1 when binary_in >= 10
14.     z <= binary_in(3) and (binary_in
        (2) or binary_in(1));
15. end PureLogic;

```

CircuitA4.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity CircuitA4 is
5.     Port (
6.         binary_in : in STD_LOGIC_VEC
            TOR(3 downto 0); --4-bit binary input
7.         z          : in STD_LOGIC; --
            Comparator result (1 if tens digit
            is 1)
8.         bcd_ones  : out STD_LOGIC_VE
            CTOR(3 downto 0) -- Adjusted BCD one
            s digit
9.     );
10. end CircuitA4;
11.
12. architecture PureLogic of CircuitA4
    is
13.     signal subtract_10 : STD_LOGIC_V
            ECTOR(3 downto 0) := "1001"; -- Bina
            ry 9
14.     signal result      : STD_LOGIC_V
            ECTOR(3 downto 0); -- Result after s
            ubtraction
15.     signal borrow      : STD_LOGIC_V
            ECTOR(4 downto 0); -- Borrow propaga
            tion
16. begin
17.     -- Borrow propagation and subtra
            ction
18.     borrow(0) <= z; -- Borrow starts
            only when z = 1
19.     result(0) <= binary_in(0) xor su
            btract_10(0) xor borrow(0);

```

```

20.     borrow(1) <= (not binary_in(0) a
            nd subtract_10(0)) or
21.         (not binary_in(0) a
            nd borrow(0)) or
22.         (subtract_10(0) and
            borrow(0));
23.
24.     result(1) <= binary_in(1) xor su
            btract_10(1) xor borrow(1);
25.     borrow(2) <= (not binary_in(1) a
            nd subtract_10(1)) or
26.         (not binary_in(1) a
            nd borrow(1)) or
27.         (subtract_10(1) and
            borrow(1));
28.
29.     result(2) <= binary_in(2) xor su
            btract_10(2) xor borrow(2);
30.     borrow(3) <= (not binary_in(2) a
            nd subtract_10(2)) or
31.         (not binary_in(2) a
            nd borrow(2)) or
32.         (subtract_10(2) and
            borrow(2));
33.
34.     result(3) <= binary_in(3) xor su
            btract_10(3) xor borrow(3);
35.
36.     -- MUX to select adjusted or una
            djusted value
37.     bcd_ones(0) <= (not z and binary
            _in(0)) or (z and result(0));
38.     bcd_ones(1) <= (not z and binary
            _in(1)) or (z and result(1));
39.     bcd_ones(2) <= (not z and binary
            _in(2)) or (z and result(2));
40.     bcd_ones(3) <= (not z and binary
            _in(3)) or (z and result(3));
41. end PureLogic;

```

CircuitB4.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity CircuitB4 is

```

```

5.     Port (
6.         z          : in STD_LOGIC; --
           Comparator result
7.         bcd_tens : out STD_LOGIC --
           Tens digit
8.     );
9. end CircuitB4;
10.
11. architecture PureLogic of CircuitB4
12. is
13.     -- Tens digit Logic
14.     bcd_tens <= z;
15. end PureLogic;

```

Char_7seg.vhd

```

1. library ieee;
2. use ieee.std_logic_1164.all;
3.
4. entity char_7seg is
5.     port (
6.         c : in std_logic_vector(3 downto 0); -- 4-bit input character code
7.         display : out std_logic_vector(7 downto 0) -- 7-segment output
8.     );
9. end char_7seg;
10.
11. architecture behavior of char_7seg is
12. begin
13.     process(c)
14.     begin
15.         case c is
16.             when "0000" => display <= "11000000"; -- 0
17.             when "0001" => display <= "11111001"; -- 1
18.             when "0010" => display <= "10100100"; -- 2
19.             when "0011" => display <= "10110000"; -- 3
20.             when "0100" => display <= "10011001"; -- 4

```

```

21.             when "0101" => display <= "10010010"; -- 5
22.             when "0110" => display <= "10000010"; -- 6
23.             when "0111" => display <= "11111000"; -- 7
24.             when "1000" => display <= "10000000"; -- 8
25.             when "1001" => display <= "10010000"; -- 9
26.             when others => display <= "11111111"; -- Default to blank
27.         end case;
28.     end process;
29. end behavior;

```

Char_7segB.vhd

```

1. library ieee;
2. use ieee.std_logic_1164.all;
3.
4. entity char_7segB is
5.     port (
6.         c : in std_logic; -- 1-bit input character code
7.         display : out std_logic_vector(7 downto 0) -- 7-segment output
8.     );
9. end char_7segB;
10.
11. architecture behavior of char_7segB is
12. begin
13.     process(c)
14.     begin
15.         case c is
16.             when '0' => display <= "11000000"; -- 0
17.             when '1' => display <= "11111001"; -- 1
18.             when others => display <= "11111111"; -- Default to blank
19.         end case;
20.     end process;
21. end behavior;

```

Part V

```
1. library ieee;
2. use ieee.std_logic_1164.all;
3. use ieee.numeric_std.all;
4.
5. entity part5 is
6. port(
7.   sw : in std_logic_vector(15 downto
8.     0);
9.   hex7, hex6, hex5, hex4, hex2, hex1,
10.   hex0 : out std_logic_vector(7 downto
11.     0)
12. );
13. end part5;
14.
15. architecture behavior of part5 is
16. signal num_one : integer := 0;
17. signal num_two : integer := 0;
18. signal num_one_tens_digit : integer
19.   range 9 downto 0 := 0;
20. signal num_one_ones_digit : integer
21.   range 9 downto 0 := 0;
22. signal num_two_tens_digit : integer
23.   range 9 downto 0 := 0;
24. signal num_two_ones_digit : integer
25.   range 9 downto 0 := 0;
26.
27. signal sum : integer := 0;
28. signal sum_hundreds_digit : integer
29.   range 9 downto 0 := 0;
30. signal sum_tens_digit : integer
31.   range 9 downto 0 := 0;
32. signal sum_ones_digit : integer
33.   range 9 downto 0 := 0;
34.
35. begin
36.
37. hex_0: entity work.char_7seg
38. Port Map(
39.   c => sum_ones_digit,
40.   display => hex0
41. );
42.
43. hex_1: entity work.char_7seg
```

```
33. Port Map(
34.   c => sum_tens_digit,
35.   display => hex1
36. );
37.
38. hex_2: entity work.char_7seg
39. Port Map(
40.   c => sum_hundreds_digit,
41.   display => hex2
42. );
43.
44. hex_4: entity work.char_7seg
45. Port Map(
46.   c => num_two_ones_digit,
47.   display => hex4
48. );
49.
50. hex_5: entity work.char_7seg
51. Port Map(
52.   c => num_two_tens_digit,
53.   display => hex5
54. );
55.
56. hex_6: entity work.char_7seg
57. Port Map(
58.   c => num_one_ones_digit,
59.   display => hex6
60. );
61.
62. hex_7: entity work.char_7seg
63. Port Map(
64.   c => num_one_tens_digit,
65.   display => hex7
66. );
67.
68. process(sw, num_one, num_two, sum)
69. begin
70.   num_one <= to_integer(unsigned(sw(
71.     15 downto 12))) * 10 + to_integer(unsigned(sw(11 downto 8)));
72.   num_two <= to_integer(unsigned(sw(
73.     7 downto 4))) * 10 + to_integer(unsigned(sw(3 downto 0)));
74.   sum <= num_one + num_two;
```

```

1.
73. -- num_one display --
74. num_one_tens_digit <= num_one / 10
   ;
75. num_one_ones_digit <= num_one mod
   10;
76.
77.
78. -- num_two display --
79. num_two_tens_digit <= num_two / 10
   ;
80. num_two_ones_digit <= num_two mod
   10;
81.
82.
83. -- sum display --
84. sum_hundreds_digit <= sum / 100;
85. sum_tens_digit <= ((sum - 100 * su
   m_hundreds_digit) - (sum - 100 * sum
   _hundreds_digit) mod 10) / 10;
86. sum_ones_digit <= sum mod 10;
87.
88. end process;
89. end behavior;

```

Char_7seg.vhd

```

1. library ieee;
2. use ieee.std_logic_1164.all;
3.
4. entity char_7seg is
5.     port (
6.         c : in integer; -- 4-bit inp
           ut character code
7.         display : out std_logic_vect
           or(7 downto 0) -- 7-segment output
8.     );
9. end char_7seg;
10.
11. architecture behavior of char_7seg i
   s
12. begin
13.     process(c)
14.     begin
15.         case c is

```

```

16.         when 0 => display <= "11
           000000"; -- 0
17.         when 1 => display <= "11
           111001"; -- 1
18.         when 2 => display <= "10
           100100"; -- 2
19.         when 3 => display <= "10
           110000"; -- 3
20.         when 4 => display <= "10
           011001"; -- 4
21.         when 5 => display <= "10
           010010"; -- 5
22.         when 6 => display <= "10
           000010"; -- 6
23.         when 7 => display <= "11
           111000"; -- 7
24.         when 8 => display <= "10
           000000"; -- 8
25.         when 9 => display <= "10
           010000"; -- 9
26.         when others => display <
           = "11111111"; -- Default to blank
27.         end case;
28.     end process;
29. end behavior;

```

Part VI

```

1. library ieee;
2. use ieee.std_logic_1164.all;
3. use ieee.numeric_std.all;
4.
5. entity part6 is
6.     port(
7.         sw : in std_logic_vector(15 downto
           0);
8.         hex7, hex6, hex5, hex4, hex2, hex1,
           hex0 : out std_logic_vector(7 downto
           0)
9.     );
10. end part6;
11.
12. architecture behavior of part6 is
13.

```

```

14. signal a, b, c, t, z : integer := 0
    ;
15. signal a_1, a_0, b_1, b_0 : integer
    range 9 downto 0 := 0;
16. signal c_2, c_1, c_0, t_1, t_0, z_1,
    z_0 : integer := 0;
17. signal s_0, s_1, s_2 : integer rang
    e 9 downto 0 := 0;
18.
19. begin
20. process(sw, a, b, c, t, z)
21. begin
22. a_1 <= to_integer(unsigned(sw(15 d
    ownto 12)));
23. a_0 <= to_integer(unsigned(sw(11
    downto 8)));
24. b_1 <= to_integer(unsigned(sw(7 do
    wnto 4)));
25. b_0 <= to_integer(unsigned(sw(3 do
    wnto 0)));
26.
27. -- algorithm given --
28. t_0 <= a_0 + b_0;
29. if t_0 > 9 then
30. z_0 <= 10;
31. c_1 <= 1;
32. else
33. z_0 <= 0;
34. c_1 <= 0;
35. end if;
36.
37. s_0 <= t_0 - z_0;
38. t_1 <= a_1 + b_1 + c_1;
39.
40. if t_1 > 9 then
41. z_1 <= 10;
42. c_2 <= 1;
43. else
44. z_1 <= 0;
45. c_2 <= 0;
46. end if;
47.
48. s_1 <= t_1 - z_1;
49. s_2 <= c_2;

```

```

50.
51. -- a display --
52. case a_1 is
53. when 0 => hex7 <= "11111111";
54. when 1 => hex7 <= "11111001";
55. when 2 => hex7 <= "10100100";
56. when 3 => hex7 <= "10110000";
57. when 4 => hex7 <= "10011001";
58. when 5 => hex7 <= "10010010";
59. when 6 => hex7 <= "10000010";
60. when 7 => hex7 <= "11111000";
61. when 8 => hex7 <= "10000000";
62. when 9 => hex7 <= "10010000";
63. end case;
64.
65. case a_0 is
66. when 0 => hex6 <= "11000000";
67. when 1 => hex6 <= "11111001";
68. when 2 => hex6 <= "10100100";
69. when 3 => hex6 <= "10110000";
70. when 4 => hex6 <= "10011001";
71. when 5 => hex6 <= "10010010";
72. when 6 => hex6 <= "10000010";
73. when 7 => hex6 <= "11111000";
74. when 8 => hex6 <= "10000000";
75. when 9 => hex6 <= "10010000";
76. end case;
77.
78. -- b display --
79.
80. case b_1 is
81. when 0 => hex5 <= "11111111";
82. when 1 => hex5 <= "11111001";
83. when 2 => hex5 <= "10100100";
84. when 3 => hex5 <= "10110000";
85. when 4 => hex5 <= "10011001";
86. when 5 => hex5 <= "10010010";
87. when 6 => hex5 <= "10000010";
88. when 7 => hex5 <= "11111000";
89. when 8 => hex5 <= "10000000";
90. when 9 => hex5 <= "10010000";
91. end case;
92.
93. case b_0 is

```

```

94.  when 0 => hex4 <= "11000000";
95.  when 1 => hex4 <= "11111001";
96.  when 2 => hex4 <= "10100100";
97.  when 3 => hex4 <= "10110000";
98.  when 4 => hex4 <= "10011001";
99.  when 5 => hex4 <= "10010010";
100. when 6 => hex4 <= "10000010";
101. when 7 => hex4 <= "11111000";
102. when 8 => hex4 <= "10000000";
103. when 9 => hex4 <= "10010000";
104. end case;
105.
106. -- sum display --
107.
108. case s_2 is
109.  when 0 => hex2 <= "11111111";
110.  when 1 => hex2 <= "11111001";
111.  when 2 => hex2 <= "10100100";
112.  when 3 => hex2 <= "10110000";
113.  when 4 => hex2 <= "10011001";
114.  when 5 => hex2 <= "10010010";
115.  when 6 => hex2 <= "10000010";
116.  when 7 => hex2 <= "11111000";
117.  when 8 => hex2 <= "10000000";
118.  when 9 => hex2 <= "10010000";
119. end case;
120.
121. case s_1 is
122.  when 0 => hex1 <= "11000000";
123.  when 1 => hex1 <= "11111001";
124.  when 2 => hex1 <= "10100100";
125.  when 3 => hex1 <= "10110000";
126.  when 4 => hex1 <= "10011001";
127.  when 5 => hex1 <= "10010010";
128.  when 6 => hex1 <= "10000010";
129.  when 7 => hex1 <= "11111000";
130.  when 8 => hex1 <= "10000000";
131.  when 9 => hex1 <= "10010000";
132. end case;
133.
134. case s_0 is
135.  when 0 => hex0 <= "11000000";
136.  when 1 => hex0 <= "11111001";
137.  when 2 => hex0 <= "10100100";

```

```

138.  when 3 => hex0 <= "10110000";
139.  when 4 => hex0 <= "10011001";
140.  when 5 => hex0 <= "10010010";
141.  when 6 => hex0 <= "10000010";
142.  when 7 => hex0 <= "11111000";
143.  when 8 => hex0 <= "10000000";
144.  when 9 => hex0 <= "10010000";
145. end case;
146. end process;
147. end behavior;

```

Part VII

Char_7seg the same as PartII

```

1.  library IEEE;
2.  use IEEE.STD_LOGIC_1164.ALL;
3.
4.  entity part7 is
5.      Port (
6.          binary_in : in STD_LOGIC_VEC
            TOR(5 downto 0); -- 6-bit binary inp
            ut
7.          hex1,hex0 : out STD_LOGIC_VECTOR(7
            downto 0)
8.      );
9.  end part7;
10.
11. architecture TruthTable of part7 is
12.
13.  -- Component declarations
14.      component char_7seg
15.          port (
16.              c : in std_logic_vector(
                3 downto 0); -- 3-bit input for th
                e character
17.              display : out std_logic_
                vector(7 downto 0) -- 7-segment outp
                ut
18.          );
19.  end component;
20.
21. signal bcd_tens : STD_LOGIC_VECTOR(
            3 downto 0);
22. signal bcd_ones : STD_LOGIC_VECTOR
            (3 downto 0);

```



```

23.
24. begin
25.     -- Map binary input to BCD tens
       digit (MSB)
26.     with binary_in select
27.         bcd_tens <=
28.             "0000" when "000000" | "
               000001" | "000010" | "000011" | "
29.             "000100" | "0
               00101" | "000110" | "000111" | "
30.             "001000" | "0
               01001",
31.             "0001" when "001010" | "
               001011" | "001100" | "001101" | "
32.             "001110" | "0
               01111" | "010000" | "010001" | "
33.             "010010" | "0
               10011",
34.             "0010" when "010100" | "
               010101" | "010110" | "010111" | "
35.             "011000" | "0
               11001" | "011010" | "011011" | "
36.             "011100" | "0
               11101" ,
37.             "0011" when "011110" | "
               011111" | "100000" | "100001" | "
38.             "100010" | "100011" | "100100"
               | "100101" | "
39.             "100110" | "100111" ,
40.             "0100" when "101000" | "
               101001" | "101010" | "101011" | "
41.             "101100" | "101101" | "101110"
               | "101111" | "
42.             "110000" | "110001" ,
43.             "0101" when "110010" | "
               110011" | "110100" | "110101" | "
44.             "110110" | "110111" | "111000"
               | "111001" | "
45.             "111010" | "111011" ,
46.             "0110" when "111100" | "
               111101" | "111110" | "111111",
47.             "0000" when others;
48.

```

```

49.     -- Map binary input to BCD ones
       digit (LSB)
50.     with binary_in select
51.         bcd_ones <=
52.             "0000" when "000000" | "
               001010" | "010100" | "011110" | "
53.             "101000" | "1
               10010" | "111100",
54.             "0001" when "000001" | "
               001011" | "010101" | "011111" | "
55.             "101001" | "1
               10011" | "111101",
56.             "0010" when "000010" | "
               001100" | "010110" | "100000" | "
57.             "101010" | "1
               10100" | "111110",
58.             "0011" when "000011" | "
               001101" | "010111" | "100001" | "
59.             "101011" | "1
               10101" | "111111",
60.             "0100" when "000100" | "
               001110" | "011000" | "100010" | "
61.             "101100" | "1
               10110",
62.             "0101" when "000101" | "
               001111" | "011001" | "100011" | "
63.             "101101" | "1
               10111",
64.             "0110" when "000110" | "
               010000" | "011010" | "100100" | "
65.             "101110" | "1
               11000",
66.             "0111" when "000111" | "
               010001" | "011011" | "100101" | "
67.             "101111" | "1
               11001",
68.             "1000" when "001000" | "
               010010" | "011100" | "100110" | "
69.             "110000" | "1
               11010",
70.             "1001" when "001001" | "
               010011" | "011101" | "100111" | "
71.             "110001" | "1
               11011",

```

```

72.         "0000" when others;
73.
74.     Hex_0: char_7seg
75.         port map (c => bcd_ones, dis
                    play => hex0);

```


```

76.
77.     Hex_1: char_7seg
78.         port map (c => bcd_tens, dis
                    play => hex1);
79.
80. end TruthTable;


```

4. Simulation and Synthesis Results

PartII

 


PartV

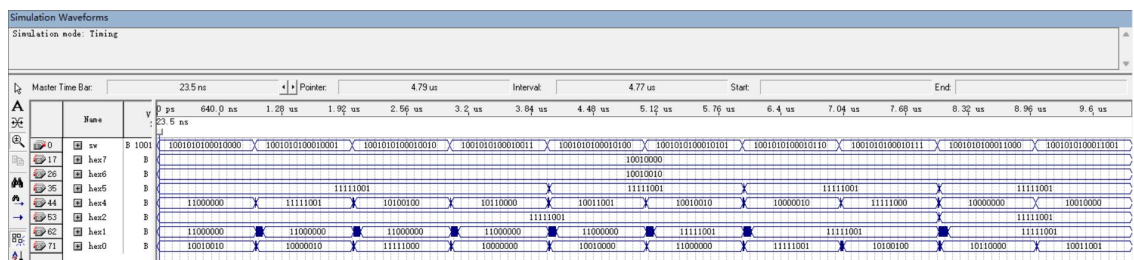


It works! Or at least I think it does...

Part VI

 


59 + 12 = 71

Part VII

 


5. Experimental Results


Part II

 


0000

 

0001

 


0111

 


1111

Part V

 


$$19 + 85 = 104$$

Part VI

 


$$98 + 87 = 185$$


Part VII

 

000111

 


011111

 

111111

 
6. Discussion and Conclusion

Nauseous as the little red dot bottom right at the HEX display screen seems, upgrading the seven-segment code to eight would help, as the oHEX_DP bit is covered. Here's the one implemented.




Looks a lot tidier and cleaner than usual. It would be a useful gag when floating-point arithmetic occurs.

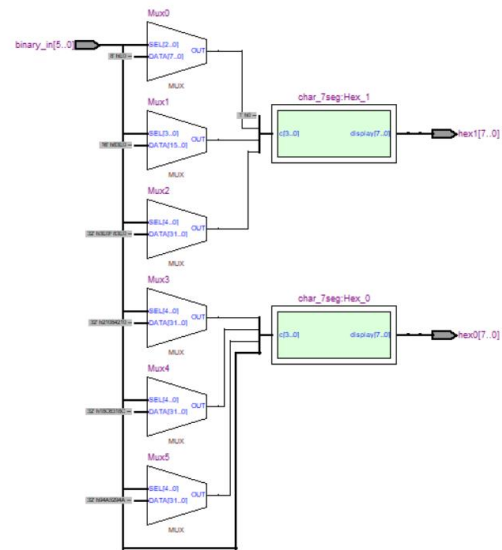
Also, there is inherently some difference between the structural implementation of 4 bit BCD converter and the purely boolean one, though not in the way that would affect hardware processing. One would be more graceful if structuring it closer to the first method for there would be naturally more portable and easily maintained.



The bad...

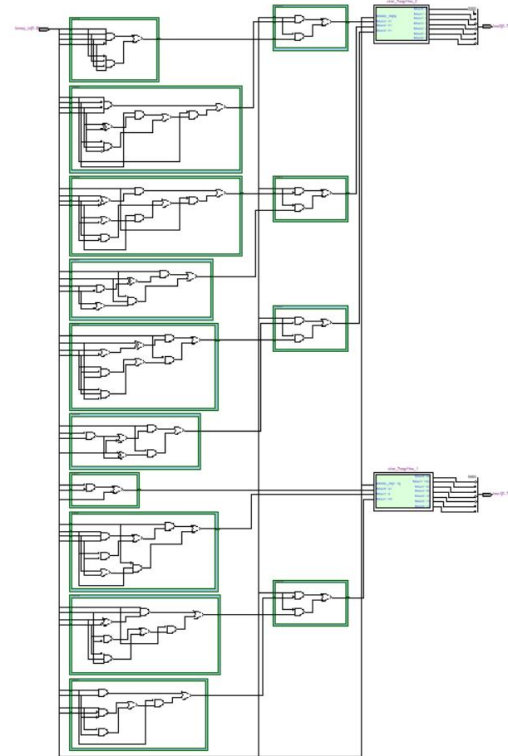

And the ugly. Both of them.

 

The good...